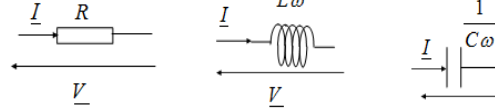



## Alternative current (AC) Sine Wave , Single-phase AC power

### RESISTOR      INDUCTOR      CAPACITOR



Impedance ( $\Omega$ )	$ Z  = R$	$ Z  = L\omega$	$ Z  = \frac{1}{C\omega}$
Phase shift (rad)	$\varphi = 0$	$\varphi = +\frac{\pi}{2}$	$\varphi = -\frac{\pi}{2}$
Complex impedance ( $\Omega$ )	$\underline{Z} = R$	$\underline{Z} = jL\omega$	$\underline{Z} = -j\frac{1}{C\omega}$
Active Power (W)	$P = RI^2$	$P = 0$	$P = 0$
Reactive Power (VAR)	$Q = 0$	$Q = L\omega I^2$	$Q = -C\omega V^2$
Apparent Power (VA)	$\underline{S} = P$	$\underline{S} = jQ$	$\underline{S} = -jQ$

### Power triangle

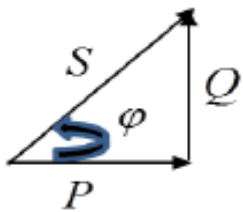

$$P = |\underline{S}| \cos \varphi$$

$$Q = |\underline{S}| \sin \varphi$$

$$|\underline{S}| = \sqrt{P^2 + Q^2}$$

### Power and Power Factor in an AC Circuit


$$P = VI \cos \varphi$$

$$Q = VI \sin \varphi$$

$$|\underline{S}| = VI$$

$$\cos \varphi = \frac{P}{S} = \frac{P}{\sqrt{P^2 + Q^2}}$$


### Impedance Combinations

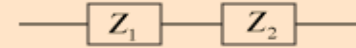

$$\begin{aligned} Z_1 + Z_2 &= (R_1 + jX_1) + (R_2 + jX_2) \\ &= (R_1 + R_2) + j(X_1 + X_2) = R_{eq} + jX_{eq} \end{aligned}$$


$$|Z| = \sqrt{R_{eq}^2 + X_{eq}^2} \quad \varphi = \tan^{-1} \frac{X_{eq}}{R_{eq}}$$
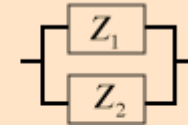
$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$



$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} \quad Z_{eq} = R_{eq} + jX_{eq} = |Z| e^{j\varphi}$$

### Simple voltage divider

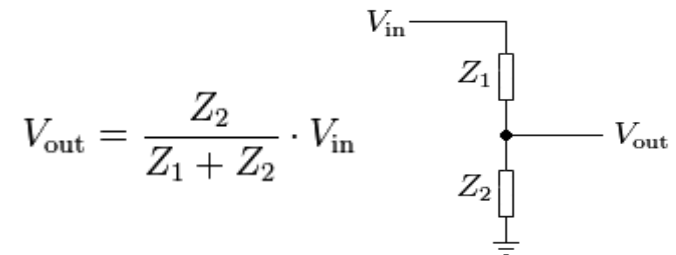

$$V_{out} = \frac{Z_2}{Z_1 + Z_2} \cdot V_{in}$$

## Alternative current (AC) Sine Wave , Single-phase AC power


### Compensation with capacities

$$Q_c = -C\omega V^2 = Q' - Q$$

$$-C\omega V^2 = P \tan \varphi' - P \tan \varphi$$

$$C = \frac{P(\tan \varphi - \tan \varphi')}{\omega V^2}$$

### Voltage drop calculations

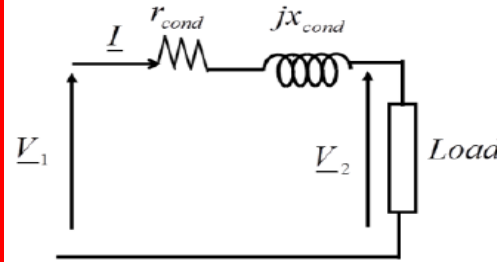

$$\underline{\Delta V} = \underline{V}_1 - \underline{V}_2$$

$$\underline{\Delta V} = \underline{Z}_{cond} \times \underline{I}$$

$$\underline{Z}_{cond} = (r_{cond} + jx_{cond})$$

$$\Delta V = r_{cond} I \cos \varphi + x_{cond} I \sin \varphi$$

### Boucherot theorem or conservation theorem for complex power

$$P = \sum_{i=1}^n P_i$$


$$Q = \sum_{i=1}^n Q_i$$

$$\underline{S} = \sum_{i=1}^n \underline{S}_i$$


$$\underline{S} = P \pm jQ = \sum_{i=1}^n P_i \pm j \sum_{i=1}^n Q_i$$

## Three-Phase AC POWER

### Three phase systems

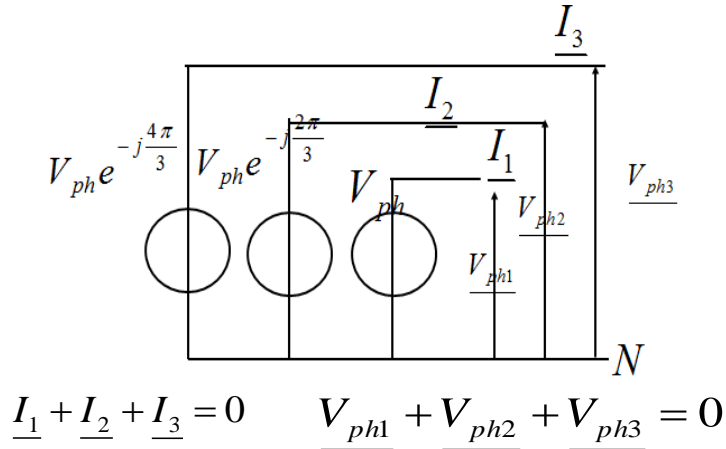


### Y configuration (Star configuration)

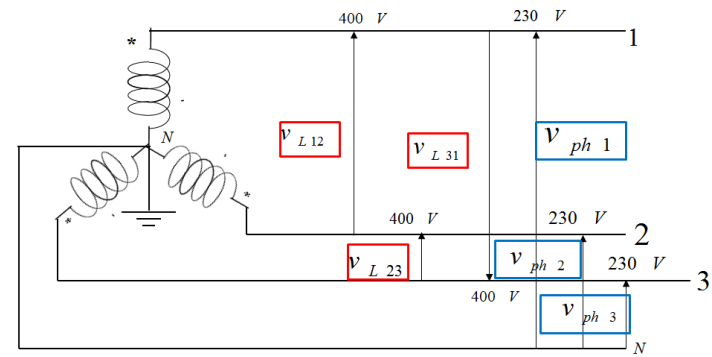

$$V_L = U = V_{ph} \sqrt{3}$$

### Delta configuration D

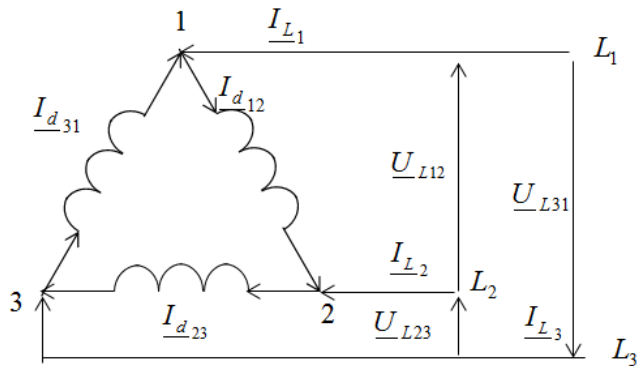

$$I_L = I_d \sqrt{3}$$


### Powers : for the two configurations

$$P = \sqrt{3} U I_L \cos \varphi$$

$$Q = \sqrt{3} U I_L \sin \varphi$$

$$S = \sqrt{3} U I_L$$



### Two-wattmeter configuration

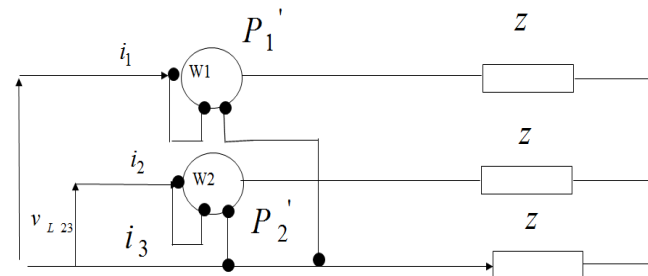

$$P = P_1' + P_2'$$

$$Q = \sqrt{3} (P_1' - P_2')$$

## Iron Core Inductor

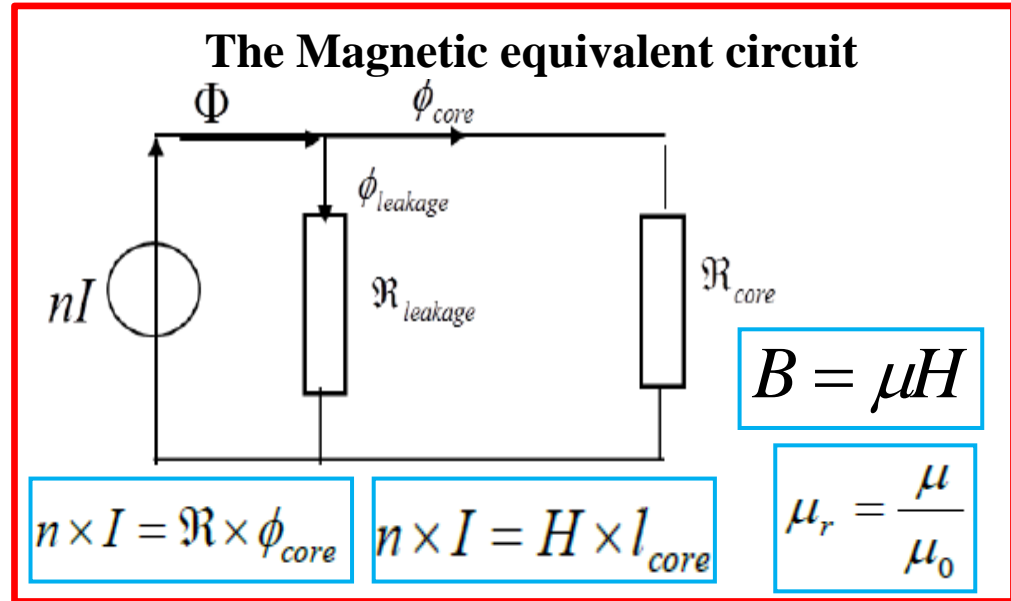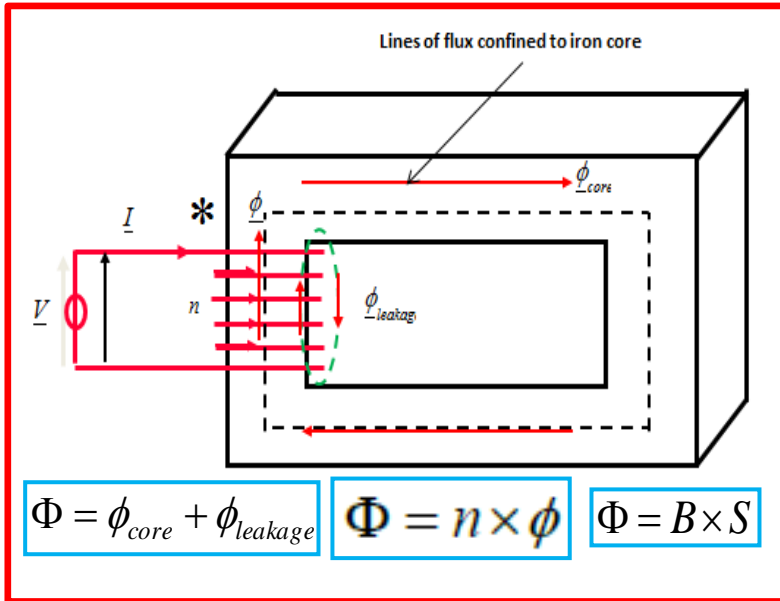

### Self inductance

$n \times I = \mathfrak{R} \times \phi$     $n \times \phi = L \times I \rightarrow \phi = \frac{L \times I}{n}$

$n \times I = \mathfrak{R} \times \frac{L \times I}{n}$     $L = \frac{n^2}{\mathfrak{R}}$

**Inductance is measured in Henry (H).**

### Inductive reactance

$X_L = L \omega = 2\pi f L$     $X_L$  is measured in (Ohm).

### Reluctance

$\mathfrak{R} = \frac{l_{core}}{\mu \times S}$    Reluctance is measured in (At/Wb).

## Iron Core Inductor

### Analogy between magnetic circuit and electric circuit

#### Magnetic Circuits

- Use Ohm's law analogy to model magnetic circuits

$$V \Leftrightarrow NI$$

$$I \Leftrightarrow \Phi$$


$$R \Leftrightarrow \mathcal{R}$$

- Use magnetic "reluctance" instead of resistance

$$R = \frac{l}{\sigma A} \Leftrightarrow \mathcal{R} = \frac{l}{\mu A}$$

Electric quantities	Magnetic quantities
Current I	Magnetic flux $\Phi$
Current density J	Magnetic flux density B
Conductivity $\sigma$	Permeability $\mu$
Electromotive force = resistance $\times$ I	Magnetomotive force = reluctance $\times$ $\Phi$
Electric field intensity E	Magnetic field intensity H
Conductance = 1/resistance	Permeance = 1/reluctance
Resistance = $l/\sigma \times S$	Reluctance = $l/\mu S$


### Magnetic system with an Air Gap

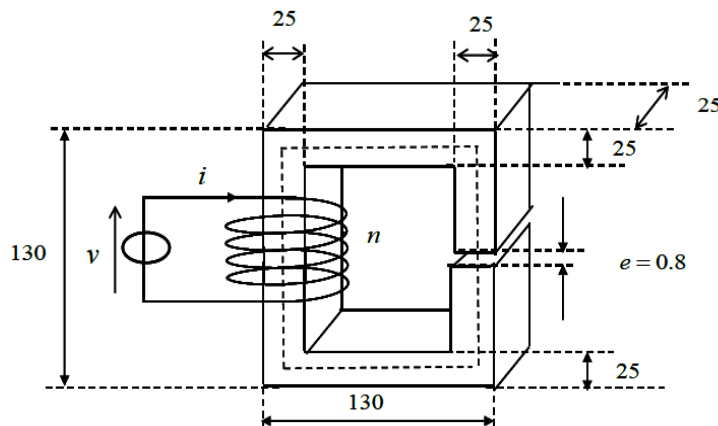

$$\mathcal{R}_{core} = \frac{l_{core}}{\mu_r \times \mu_0 \times S}$$



$$\mathcal{R}_{gap} = \frac{l_{gap}}{\mu_0 \times S}$$

The Magnetic equivalent circuit is:

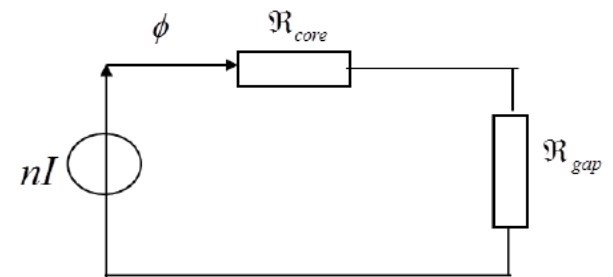

$$nI = \phi(\mathcal{R}_{core} + \mathcal{R}_{gap})$$

## A single phase transformer

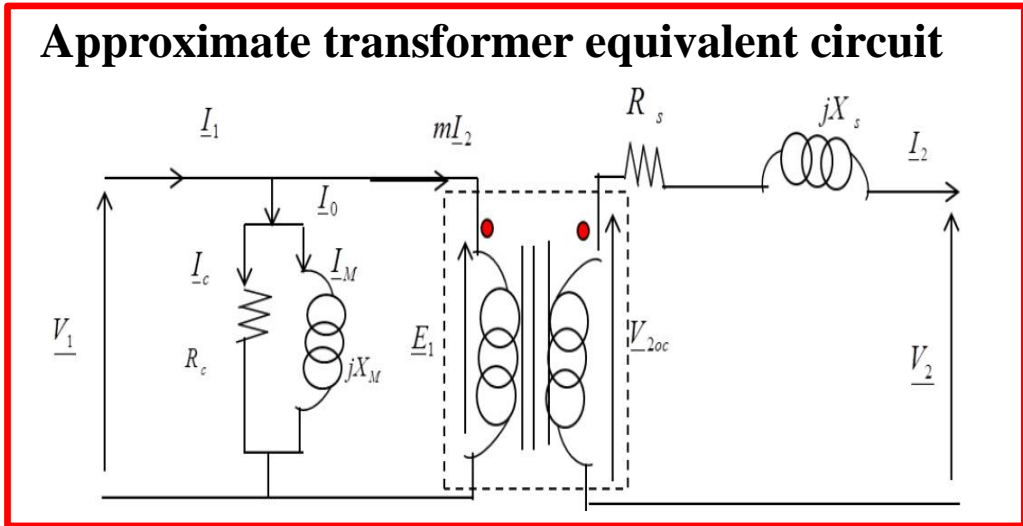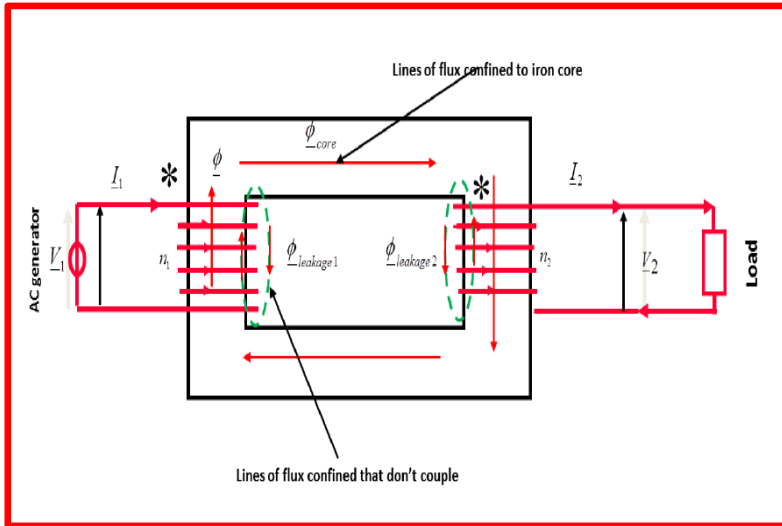

### 1. Open circuit test

- Performed at **rated voltage**
- Determines **shunt components**

$$m = \frac{n_2}{n_1} = \frac{V_{2oc}}{V_1}$$

$$R_c = \frac{V_1^2}{P_{oc}}$$

$$X_M = \frac{V_1^2}{Q_M}$$

$$S_{1oc} = V_1 I_{oc}$$

$$Q_M = \sqrt{S_{1oc}^2 - P_{oc}^2}$$

### 2. Short circuit test

- Performed at **rated current**
- Determines **series components**

$$Z_s = \frac{V_{2sc}}{I_{2sc}}$$

$$R_s = \frac{P_{sc}}{I_{2sc}^2}$$

$$X_s = \frac{Q_{sc}}{I_{2sc}^2} = \sqrt{Z_s^2 - R_s^2}$$

$$S_{1sc} = V_{1sc} I_{1sc}$$

$$Q_{sc} = \sqrt{S_{1sc}^2 - P_{sc}^2}$$




### Phase displacement

Phase rotation is always counterclockwise (internationally adopted convention) and indicates multiples of 30 degree lag for secondary winding using the primary winding as the reference.

Thus 1 = 30°, 2 = 60°, 3 = 90°, 4 = 120°, 5 = 150°, 6 = 180°, 7 = 210°, 8 = 240°, 9 = 270°, 10 = 300°, 11 = 330° and 12 = 0° or 360°.

$$n = \frac{\theta}{30^\circ}$$

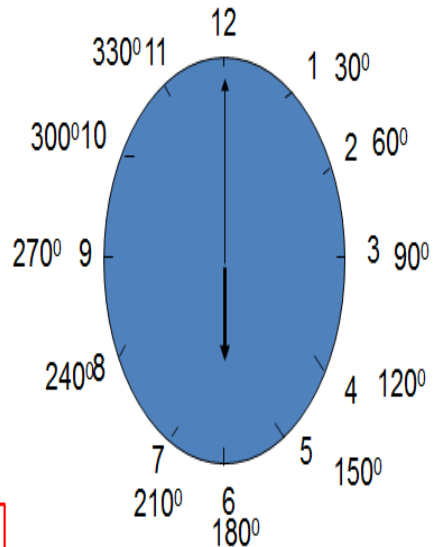


$$n = \frac{180^\circ}{30^\circ} = 6$$

$$\overline{V}_a = m e^{-j\pi} \overline{V}_A$$

Application of Transformer according to Uses: Yy<sub>0</sub>, Yd<sub>11</sub>, Dy<sub>11</sub>, Dd<sub>0</sub>

# Basic notions
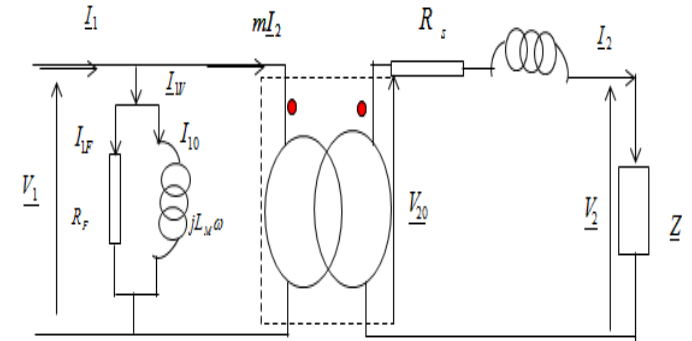
### Single-phase equivalent circuit of 3 phase transformers



$$m = \frac{U_{20}}{U_1} \quad R_F = \frac{U_1^2}{P_{IV}} \quad L_M \omega = \frac{U_1^2}{Q_{IV}} \quad Q_{IV} = \sqrt{S_{IV}^2 - P_{IV}^2} \quad S_{IV} = \sqrt{3} U_1 I_{IV}$$

$$R_s = \frac{P_{\alpha\alpha}}{3 \times I_{2cc}^2} \quad l_s \omega = \frac{Q_{\alpha\alpha}}{3 \times I_{2cc}^2} \quad Q_{\alpha\alpha} = \sqrt{S_{1cc}^2 - P_{\alpha\alpha}^2} \quad S_{1cc} = \sqrt{3} U_{1cc} I_{1cc}$$

### Voltage drop calculations

$$\Delta U_2 = \sqrt{3} (R_s I_2 \cos \varphi_2 + l_s \omega I_2 \sin \varphi_2)$$

### Efficiency

$$\eta = \frac{P_{sortie}}{P_{entrée}} = \frac{\sqrt{3} U_2 I_2 \cos \varphi_2}{\sqrt{3} U_2 I_2 \cos \varphi_2 + P_{IV} + 3 \times R_s \times I_{2cc}^2}$$