

**Exercise: Synchronous machine alternator:
Study of the power supply of an Airbus A320**

In flight, the electrical generation is ensured by two main alternators of **90 kVA** which deliver a three-phase system of voltages **115V / 200V, 400Hz**. The frequency is **kept constant** thanks to a hydraulic regulation of the rotation speed of the alternators.

We are interested in studying the **unsaturated alternator**.

The aircraft's electrical system is powered in **400 Hz**.

For the Airbus A320 the manufacturer gives:

Rated voltage V_N/U_N	115 V / 200 V
Number of phases	3
Rated apparent power S_N	90 kVA
Rated frequency f_N	400 Hz
Rated rotation speed n_N	12.0×10^3 rpm
Power factor	$0.75 < \cos\varphi < 1$
Armature resistance (per phase) R_s	10 mΩ

The armature is **star-coupled**.

Two tests were performed at constant rated speed: **n_N** .

- **Generator at no-load test:** no-load characteristic $E_o(I_e)$ where E_o is the value of induced electromotive force at no load in one winding and I_e the intensity of the inductive current. The characteristic is a **straight line** such that for **$I_e=0$ corresponds $E_o = 0$** and for **$I_e=92$ A corresponds $E_o = 400$ V**.

- **Short-circuit test:** in the useful range, the short-circuit characteristic is the line with equation **$I_{sc} = 3.07 \times I_e$** , where I_{sc} is the rms value of the short-circuit current in a stator winding.

1- We are interested in **nominal operation**:

- a) Calculate the pulsation of the output voltages of the alternator.
- b) Determine the number of pole pairs of the machine.
- c) Calculate the rms value of the nominal armature current I_N .

2- We assume the alternator unsaturated.

- a) Draw its equivalent model by phase represented.
- b) Calculate the synchronous impedance of the alternator Z_s .
- c) Deduce the synchronous reactance $X_s = L_s \omega$.

3- **In the rest of the problem, the influence of stator resistance R_s is neglected.**

a) Determine the intensity of the inductive current I_{e0} for no-load operation at rated (nominal) voltage $V=115 \text{ V}$.

b) We consider a balanced three-phase load. The alternator operates **in nominal conditions**; it delivers its rated current I_N , **behind** (“en retard”) the voltage.

For $\cos\phi = 0.75$, represent the vector diagram of the voltages and deduce:

- the value of the e.m.f induced E_0 .
- the new value of the excitation current I_e for maintaining $V = 115 \text{ V}$ at $\cos\phi = 0.75$ when the alternator delivers its nominal current I_N .

Correction

1)


a) $\omega = 2\pi f = 25.1 \times 10^2 \text{ rd/s}$

b) $\Omega = \frac{\omega}{p} \rightarrow p = 2$

c) $S_n = 3 V_n I_n = \sqrt{3} \times U_n \times I_N \rightarrow I_N = \frac{90 \cdot 10^3}{3 \times 115} = 260 \text{ A}$

2)

a)

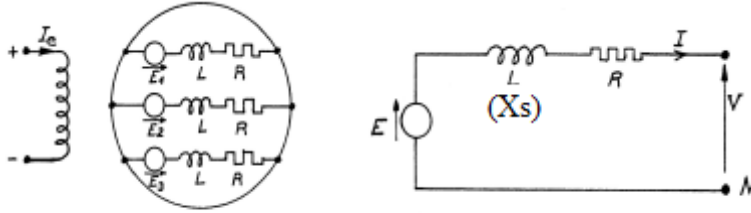

Equivalent circuit of the synchronous machine

b) $\underline{V} = \underline{E}_V - \underline{Z}_s \cdot \underline{I}$ et $\underline{Z}_s = \frac{E_{VCC}}{I_{CC}}$

The voltage E_V evolves linearly with I_e and its equation is : $E_V = \frac{400}{92} I_e$

And $I_{CC} = 3.07 \times I_e$

$$\underline{Z}_s = \frac{E_{VCC}}{I_{CC}} = \frac{\frac{400}{92} I_e}{3.07 \times I_e} = \frac{400}{92 \times 3.07} = 1.4 \Omega$$

c) $X_s = \sqrt{Z_s^2 - R_s^2} \approx 1.4 \Omega$

3)

a) For no-load operation at rated (nominal) voltage $V=115 \text{ V}$.

$$V = E_v = 115 \text{ V}$$

$$E_v = \frac{400}{92} I_e \quad \text{so} \quad I_e = \frac{92}{400} 115 = 26.5 \text{ A}$$

b) $V_n = 115 \text{ V}$

$$X_s I_N = 1.4 \times 260 = 364 \text{ V}$$


$$\cos \varphi = 0.75 \rightarrow \varphi_{V/II} = 41.5^\circ$$

On the diagram we read: $E_V = 450 \text{ V}$

We can verify by calculation:

$$E_V = \sqrt{(V \cos \varphi)^2 + (V \sin \varphi + X_s I)^2}$$
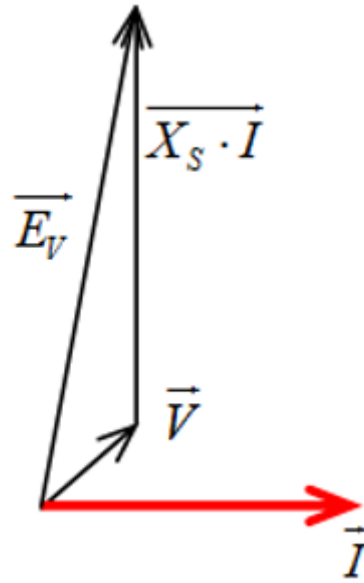
$$E_V = \sqrt{(115 \cos 41.5)^2 + (115 \sin 41.5 + 364)^2} = 448 \text{ V}$$



$$E_V = 450 \text{ V}$$

$$E_V = \frac{400}{92} I_e \text{ so } I_e = \frac{92}{400} 450 = 102 \text{ A}$$