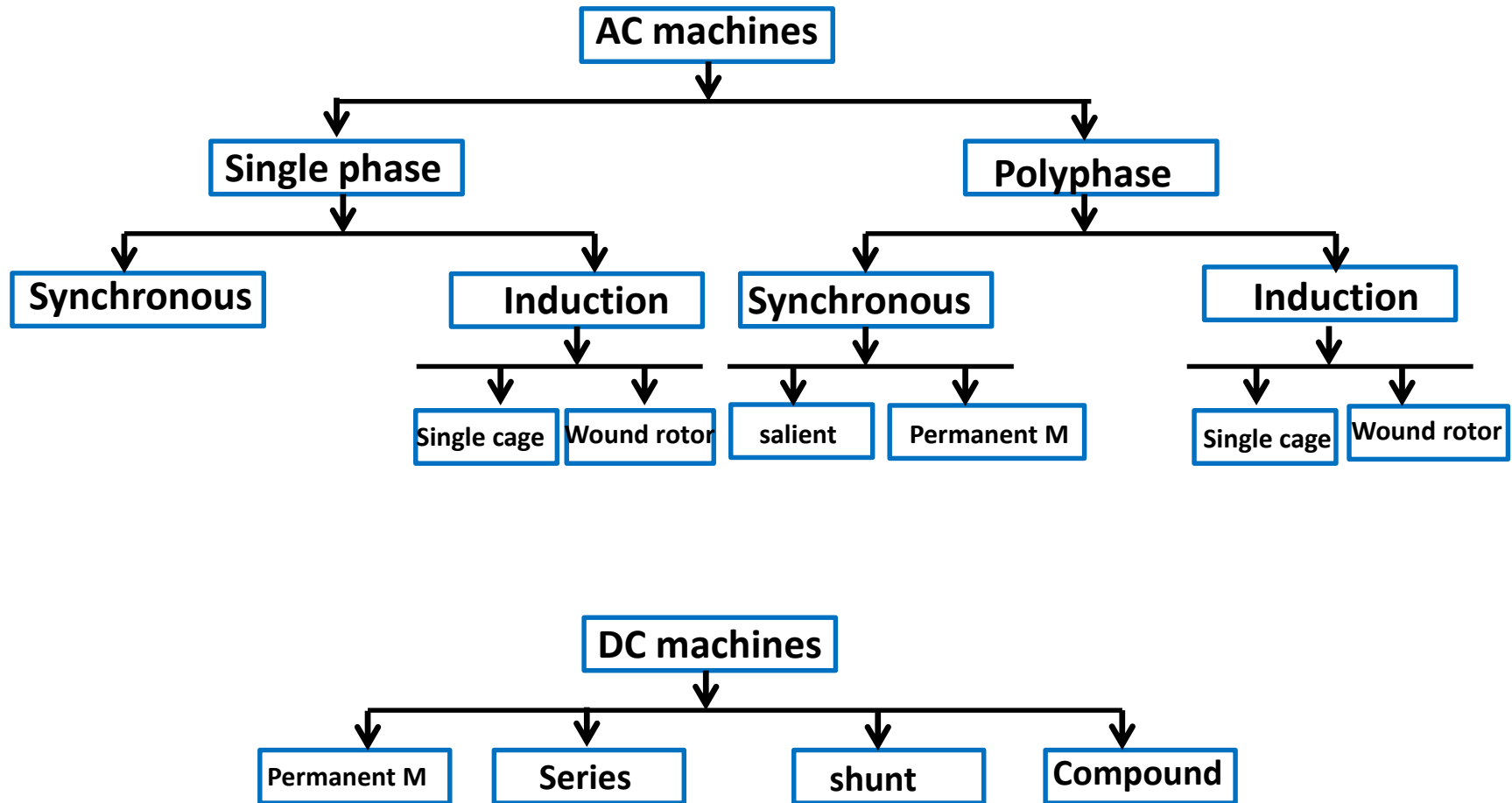


# Classification of electrical machines




# CHAPTER TWO

## DC machines


- ✓ Understand the basic principles of operation of a DC motor.
- ✓ Understand the operation and basic characteristics of simple DC motors.
- ✓ Compute electrical and mechanical quantities using the equivalent circuit.
- ✓ Study some applications of DC motors.
- ✓ Use motor nameplate data.

# Production of induced force on a wire.

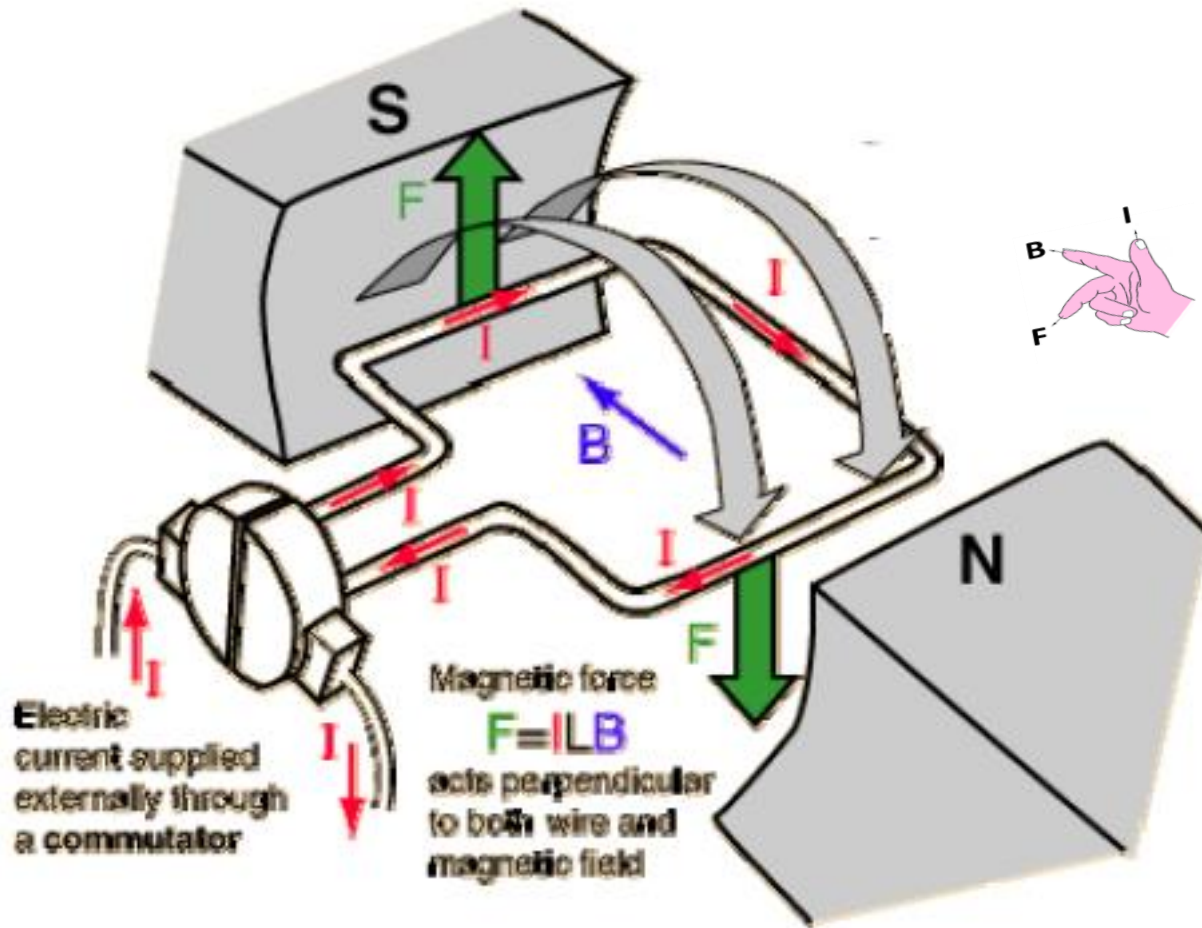

$$F = i.(l \times B)$$
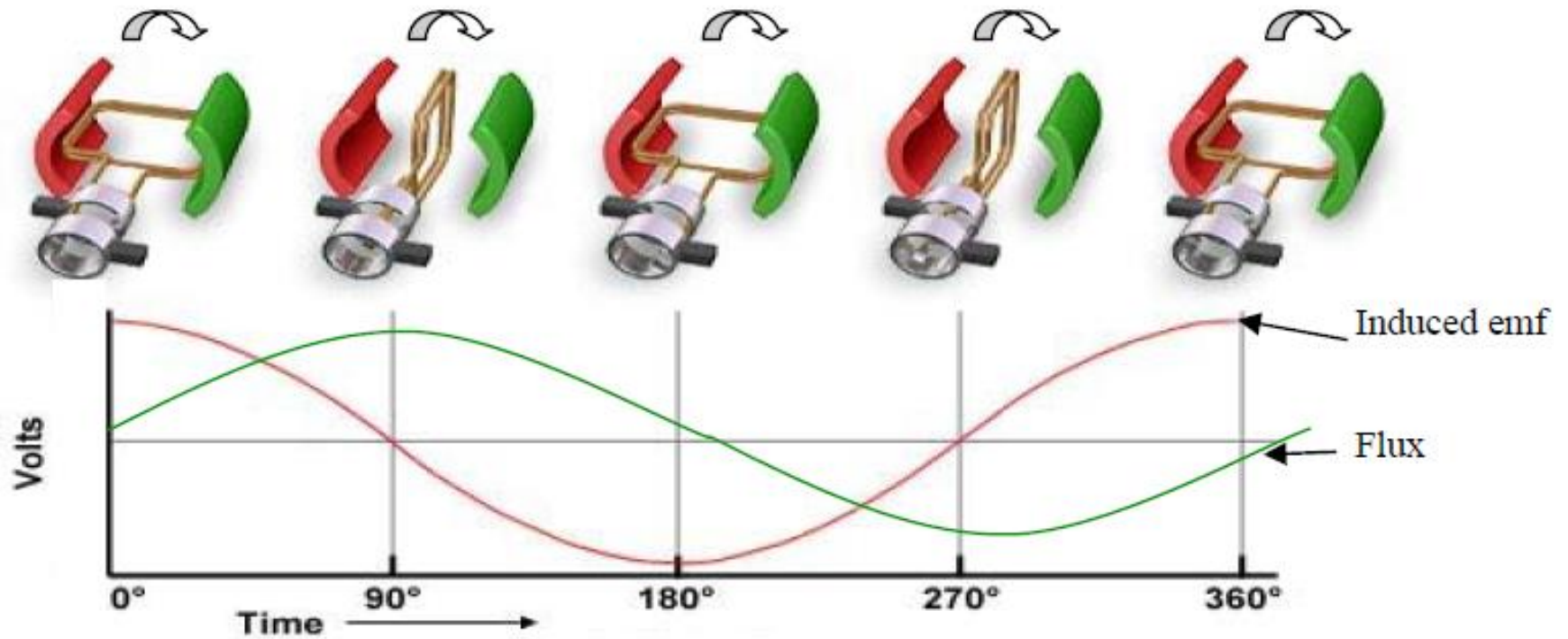
## Induced voltage in the armature winding of DC motor



# Dc motor stator construction




Moteur lève vitre

Moteur lève-vitre



Moteur universel

Moteur universel

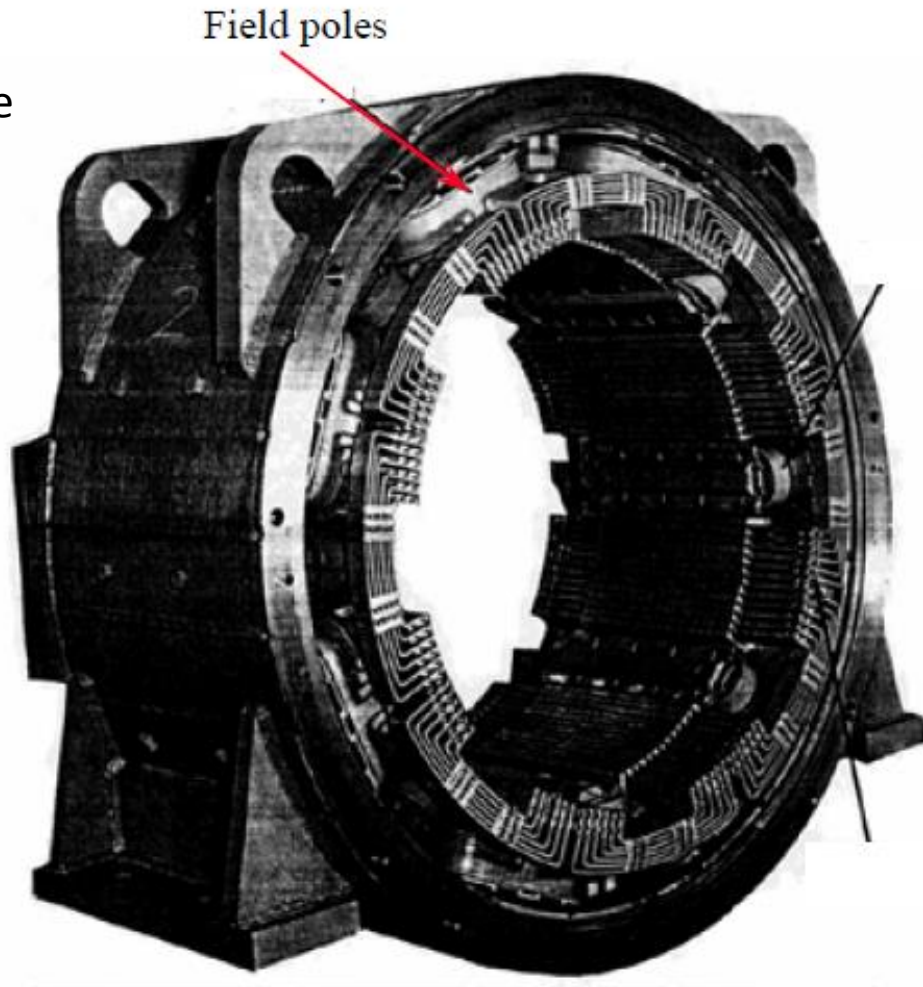


Field poles



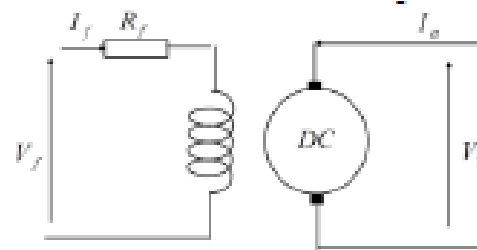
# Classification of DC motors


Separately excited: Field and armature are either connected separate



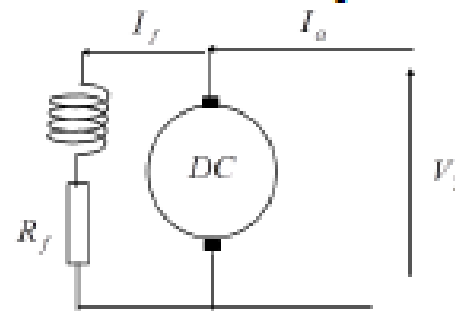
Shunt excited: Field and armature are either connected in parallel



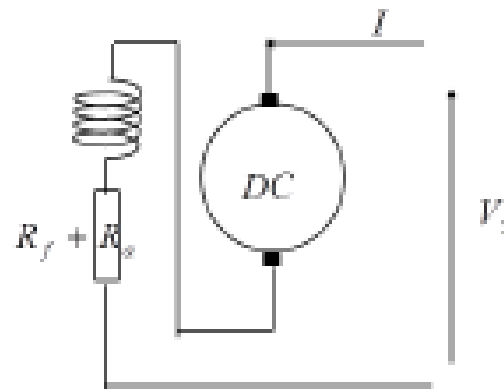Series excited: Field and armature are either connected in series



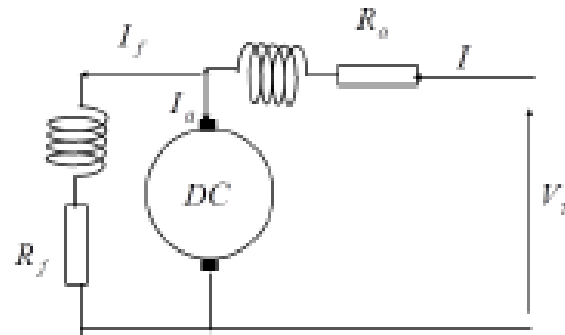Compound excited: Has both shunt and series field so it combines features of series and shunt motors.





## DC Generator Fundamentals


The voltage out of the armature of a DC generator is:  $E_A = k_1 \times \phi \times \Omega$

if the iron core is not saturated:  $\phi = k_2 I_F$

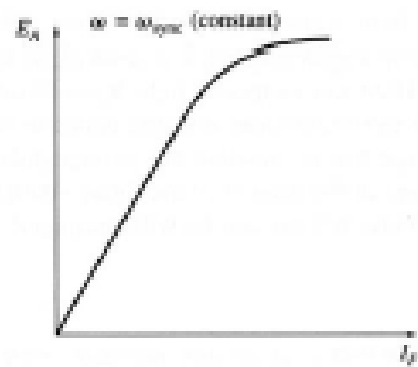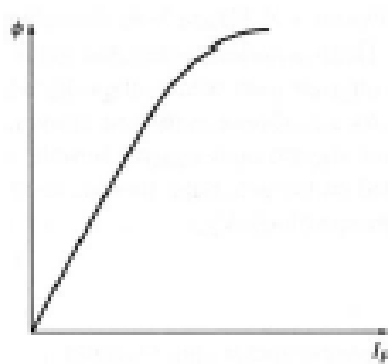Hence  $E_A = k_1 k_2 I_F \Omega = k_\phi \Omega$




## DC Generator Equivalent circuit

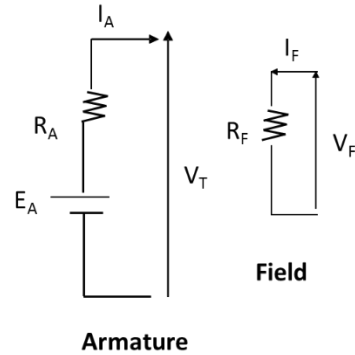

### Voltage equation:

$$E_g = V_T + R_A I_A \quad V_F = R_F \times I_F$$

## DC Motor Equivalent circuit

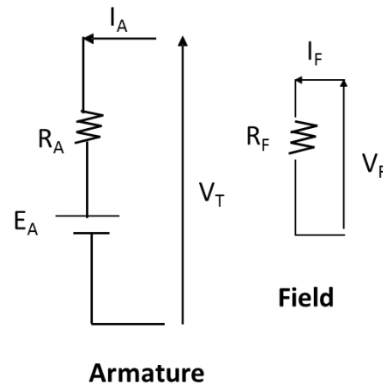

### Voltage equation:

$$V_T = E_A + R_A I_A \quad V_F = R_F \times I_F$$

## The relationship between the induced EMF and torque

$$E = Blv$$

$$T = Bli r$$

$$\frac{E_A}{T_{dev}} = \frac{Blv}{Bli r} = \frac{v}{i \times r} = \frac{\Omega \times r}{i \times r} = \frac{\Omega}{I_A}$$

$$E_{em} I_A = T_{dev} \Omega$$

$$T_{dev} = \frac{E_A \times I_A}{\Omega} = \frac{k_1 \phi \Omega I_A}{\Omega} = k_1 \phi I_A = k_e I_A$$

## The power flow and losses in DC machines

$$P_{out} = P_{in} - \sum losses$$

$\sum losses$  = Copper losses (armature and field) + Core losses (both core) + Mechanical losses

### Efficiency

Total electrical input power  $P_{in} = V_T I_A + V_F I_F$

Power absorbed by the field winding is in turn converted to heat and is given by:

$$P_f = R_F I_F^2 = R_F \left( \frac{V_F}{R_F} \right)^2 = \frac{V_F^2}{R_F}$$

Some power is lost in the resistance of the armature winding, and can be calculated as:

$$P_A = R_A I_A^2$$


$$\sum \text{copper loss} = \text{Field loss} + \text{armature loss}$$

$$P_{dev} = P_m - \sum \text{copper loss}$$

$$P_{dev} = E_A I_A = T_{dev} \Omega$$

$$P_{out} = P_{dev} - P_{rot}$$


### The power flow diagram

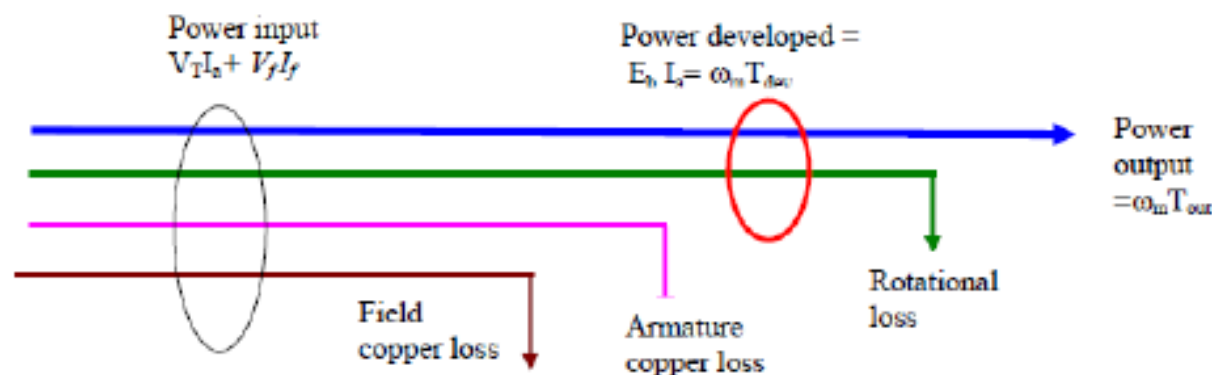

The efficiency of the DC motor can be calculated as:

$$\eta = \frac{P_{out}}{P} \times 100\%$$
$$\eta = \frac{P_{out}}{P_{out} + p_A + p_F + p_{rot}}$$

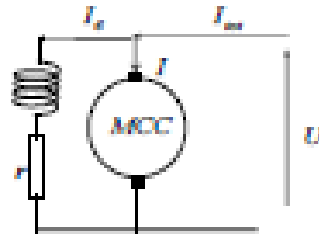**Exercise 1.** A DC shunt motor runs at no load speed 1140 rpm. At full load, armature reaction weakens the main flux by 5% whereas the armature circuit voltage drops by 10%. Calculate the motor full load speed  $N_2$  in rpm.



**Answer:**

$$E_{A1} = k_1 \phi_1 \Omega_1 \rightarrow k_1 = \frac{E_{A1}}{\phi_1 \Omega_1}$$

$$E_{A2} = k_1 \phi_2 \Omega_2 \rightarrow k_1 = \frac{E_{A2}}{\phi_2 \Omega_2}$$

$$\Omega_1 = \frac{2\pi N_1}{60}; \Omega_2 = \frac{2\pi N_2}{60} \rightarrow \frac{\Omega_2}{\Omega_1} = \frac{N_2}{N_1}$$

$$\phi_2 = 0,95 \phi_1$$

$$E_{A2} = 0,9 E_{A1}$$

$$\frac{E_{A1}}{\phi_1 N_1} = \frac{E_{A2}}{\phi_2 N_2}$$

$$\frac{E_{A1}}{\phi_1 N_1} = \frac{0,9 E_{A1}}{0,95 \phi_1 N_2} \quad \frac{1}{N_1} = \frac{0,9}{0,95 N_2} \quad N_2 = \frac{0,9 N_1}{0,95} = 1080 \text{ rpm}$$

## Exercise2

A DC machine has a flux per pole of  $30 \cdot 10^{-3}$  Wb. The DC machine runs at 1050 rpm and it delivers a rated armature current of 225 A to a load connected to its terminals, the machine constant  $K_1 = 85,21$ . Calculate:

- A) Generated voltage,  $E_A$
- B) Torque developed  $T_{dev}$ .
- C) Power developed by the machine  $P_{dev}$ .

### Solution

- A) Generated voltage,  $E_A$

$$E_G = k_1 \times \phi \times \Omega$$

$$\Omega = \frac{2\pi N}{60} = \frac{2\pi \times 1050}{60} = 109,96 \text{ rad/sec}$$

$$E_A = k_1 \times \phi \times \Omega = 85,21 \times 0,03 \times 109,96 = 281 \text{ V}$$

- B) Torque developed  $T_{dev}$ .

$$T_{dev} = k_1 \times \phi \times I_A = 85,21 \times 0,03 \times 225 = 575,16 \text{ Nm}$$

- C) Power developed by the machine  $P_{dev}$ .

$$P_{dev} = E_A \cdot I_A = 281 \times 225 = 63,22 \text{ kW}$$

## Review

1. A commutator in a DC machine
  - a) Reduces power loss in armature
  - b) Reduces power loss in circuit
  - c) **Converts the induce AC armature voltage into direct voltage**
  - d) It is not necessary
2. The DC series motor should always be started with load because
  - e) **At no load, it will rotate at dangerously high speed**
  - f) It will fail to start
  - g) It will not develop high starting torque
  - h) All are true
3. In a DC series motor the developed torque is proportional to:
  - a)  $I_A$
  - b)  $I_A^2$
  - c)  $\frac{1}{I_A}$
  - d)  $\frac{1}{I_A^2}$
4. In a DC machine, the armature mmf is:
  - a) Stationary with respect to armature
  - b) Rotating with respect to field
  - c) **Stationary with respect to field**
  - d) Rotating with respect to brushes
5. The torque, in a..... is proportional to the square of armature current
  - a) DC shunt motor
  - b) Stepper motor
  - c) Two phase servomotor
  - d) **DC series motor**

## Exercise 1 Fill in the blanks

1. Coils with several turns are placed in the \_\_\_\_\_.
2. The distance between the two legs of the coil is about \_\_\_\_\_.
3. The coils are connected \_\_\_\_\_ through the commutator segments.
4. The ends of each coil are connected to a \_\_\_\_\_ segment.
5. The commutator consists of insulated \_\_\_\_\_ segments mounted on an insulated tube.
6. Two brushes are pressed to the commutator to permit \_\_\_\_\_.
7. The brushes are placed in the \_\_\_\_\_, where the magnetic field is close to zero, to reduce arcing.

## Answer

1. Slots.
2. 180 electric degrees.
3. in series
4. Commutator.
5. Copper
6. Current flow.
7. Neutral zone

*The End*