


# CHAPTER FIVE

## A single-phase transformer


### Learning Outcomes:

- Explain the production of eddy current losses within the core, and the constructional features that reduce them
- Calculate applied voltage and induced voltage.
- Draw and label both the full equivalent circuit and the simplified equivalent transformer circuit
- Calculate equivalent resistance and reactance
- Calculate equivalent circuit parameters from open and short circuit test results.
- Calculate transformer efficiency for full load and half load, each with different power factors

# A single-phase transformer

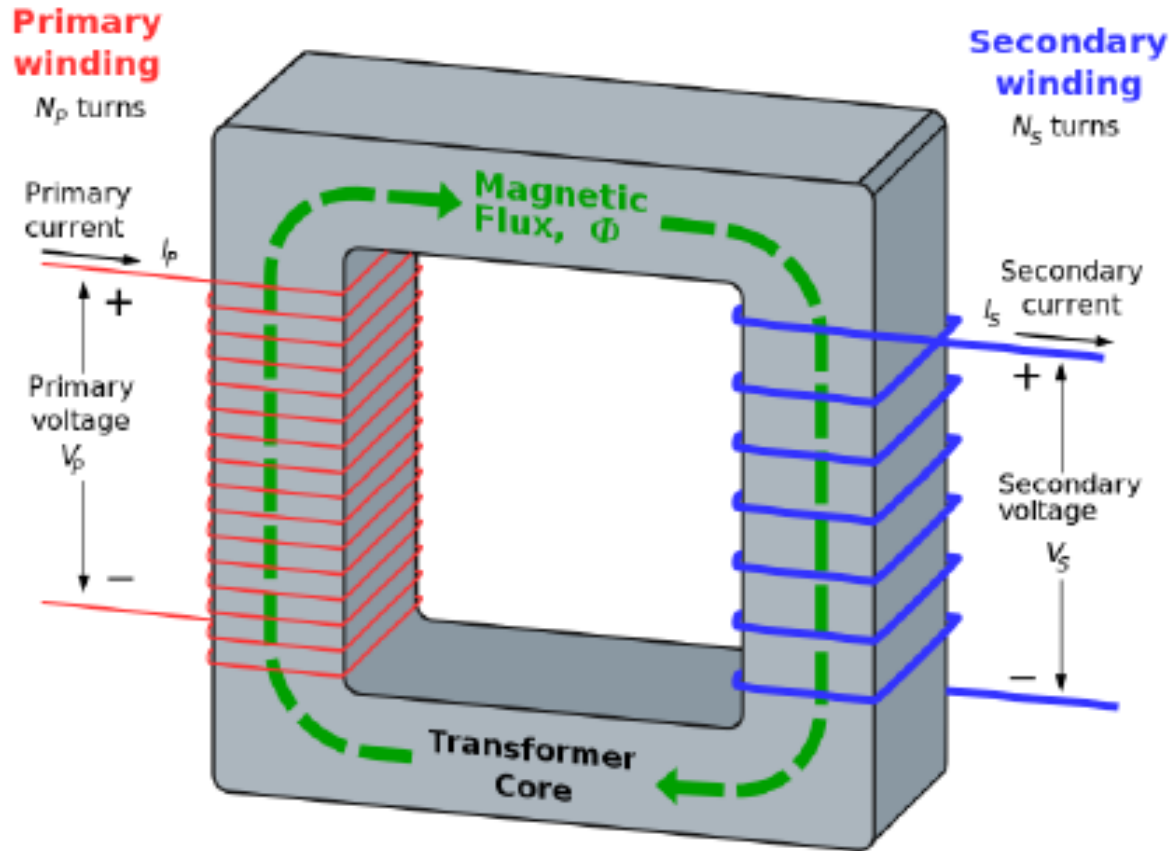

# A single-phase transformer

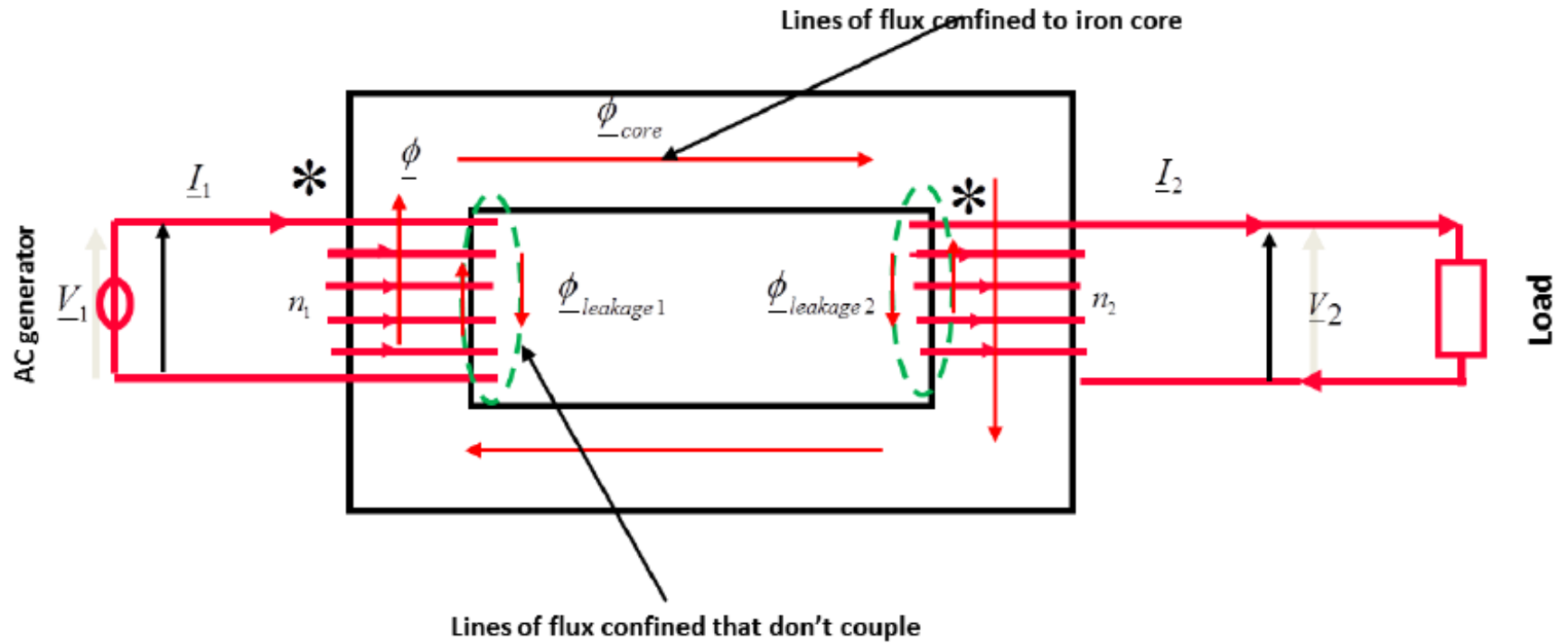

## Ideal transformer

- The windings of the transformer have no resistance. Thus, there is no copper loss in the winding, and hence no voltage drop.
- Flux is confined within the magnetic core. Therefore, it is the same flux that links the input and output windings.
- Permeability of the core is infinitely high which implies that net mmf (amp-turns) must be zero (otherwise there would be infinite flux) hence  $I_1 n_1 - I_2 n_2 = 0$ .
- The transformer core does not suffer magnetic hysteresis or eddy currents, which cause inductive loss.


$$\frac{V_2}{V_1} = \frac{n_2}{n_1} = m$$

$m$  : is the winding **turns ratio**, the value of these ratios being respectively higher and lower than unity for step-down and step-up transformers

$V_1$  : designates **input** voltage,

$V_2$  : designates **output** voltage

## Ideal transformer

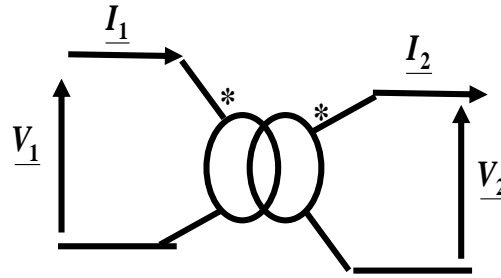

$$\mathbf{P}_1 = \mathbf{P}_2$$

$$\underline{V}_1 \underline{I}_1 = \underline{V}_2 \underline{I}_2$$

$$\frac{V_2}{V_1} = \frac{I_1}{I_2}$$

$$l_1 = l_2 = 0 ;$$

$$r_1 = r_2 = 0$$


$$\mathcal{R} = 0 ;$$

$$R_F = 0$$

$$\frac{\underline{V}_2}{\underline{V}_1} = \frac{\underline{I}_1}{\underline{I}_2} = \frac{n_2}{n_1}$$

$$n_1 \underline{I}_1 - n_2 \underline{I}_2 = 0$$


$$\frac{n_2}{n_1} = \frac{I_1}{I_2}$$

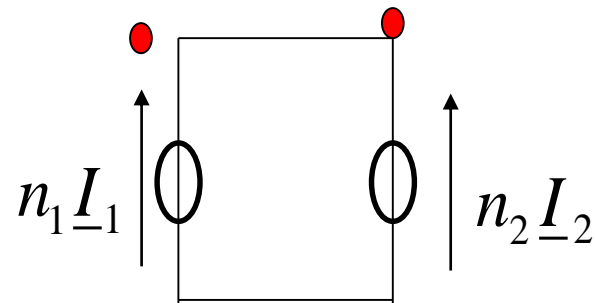

## Real transformer

- Joule losses due to resistance in the primary and secondary windings
- Hysteresis losses due to nonlinear application of the voltage applied in the transformer core,
- Eddy current losses due to joule heating in the core that are proportional to the square of the transformer's applied voltage.
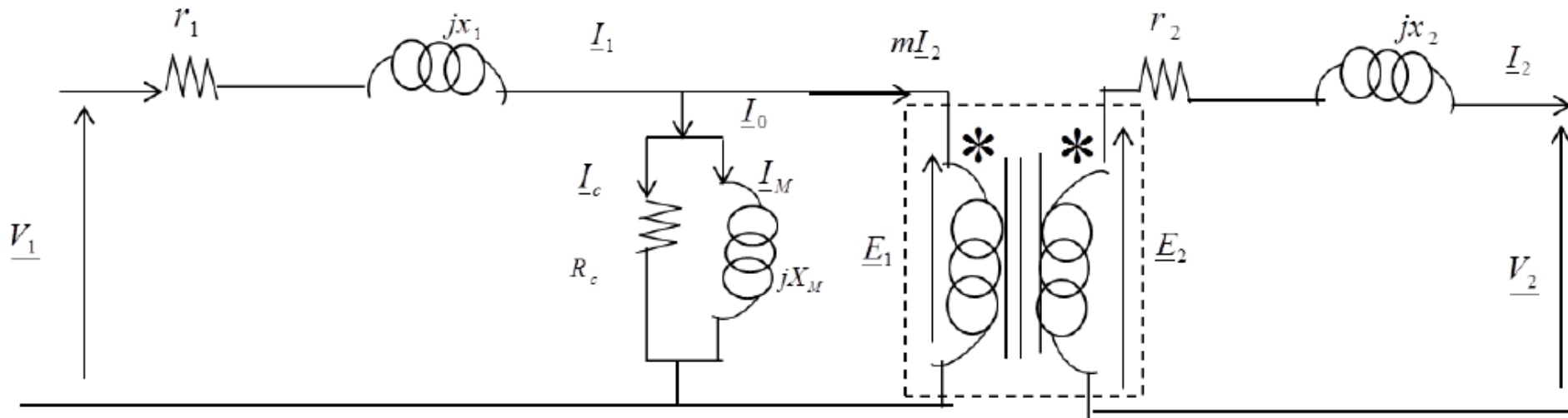
## Equivalent circuit of real transformer




### Phenomena not covered in the equivalent circuit

- Saturation
- Inrush current
- Sinusoidal exciting current

- Resistance and reactance of primary winding:  $r_1, X_1$
- Resistance and reactance of secondary winding:  $r_2, X_2$ .
- Primary induced voltage:  $E_1$
- Secondary induced voltage:  $E_2$
- Primary terminal voltage:  $V_1$
- Secondary terminal voltage:  $V_2$
- Primary current:  $I_1$
- Secondary current:  $I_2$
- No load primary current:  $I_0$
- Magnetizing current:  $I_M$
- Current accounting for the core losses:  $I_C$
- Core or iron losses:  $R_C$
- Magnetizing reactance:  $X_M$ .
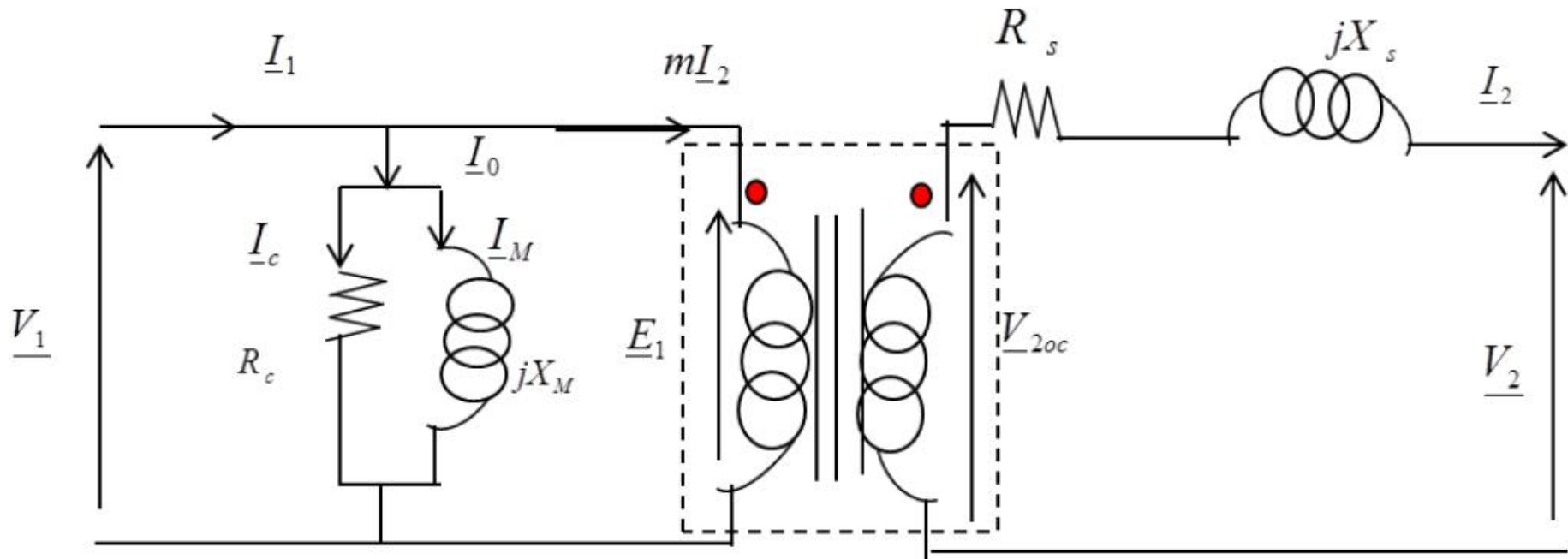
## Approximate transformer equivalent circuit



$R_s$  : Equivalent resistance transferred to secondary side.

$X_s$  : Equivalent reactance transferred to secondary side.

$Z_s$  : Equivalent impedance is transferred to secondary side.

$$R_s = r_2 + m^2 r_1$$


$$X_s = x_2 + m^2 x_1$$

$$Z_s = R_s + jX_s$$

# Determining transformer parameters
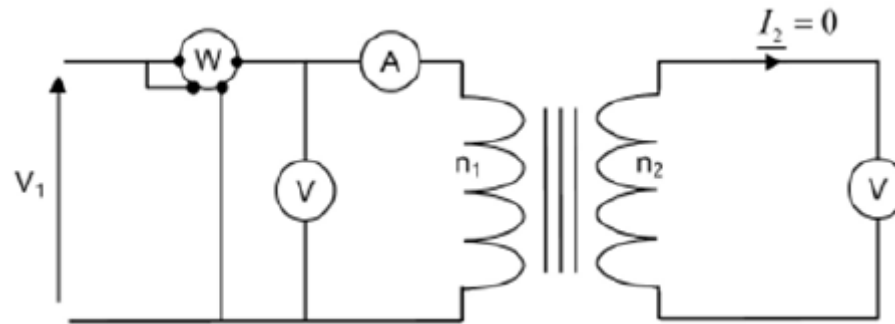
## 1. Open circuit test

- Performed at **rated voltage**
- Determines **shunt components**



$$m = \frac{n_2}{n_1} = \frac{V_{2oc}}{V_1}$$

$$R_C = \frac{V_1^2}{P_{oc}}$$


$$X_M = \frac{V_1^2}{Q_M}$$

$$Q_M = \sqrt{S_{1oc}^2 - P_{OC}^2}$$

$$S_{1oc} = V_1 I_{0c}$$
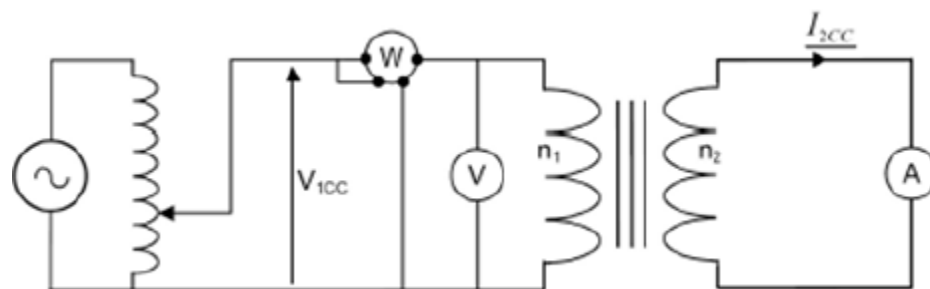
## 2. Short circuit test

- Performed at **rated current**
- Determines **series components**



$$Z_s = \frac{V_{2sc}}{I_{2sc}}$$

$$R_s = \frac{P_{sc}}{I_{2sc}^2}$$

$$X_s = \frac{Q_{sc}}{I_{2sc}^2} = \sqrt{Z_s^2 - R_s^2}$$

$$Q_{sc} = \sqrt{S_{1sc}^2 - P_{sc}^2}$$

$$S_{1sc} = V_{1sc} I_{1sc}$$



## Transformer Formulas

$$V_{2oc} = \frac{I_1}{I_2} \times V_1$$

$$m = \frac{n_2}{n_1} = \frac{V_{2oc}}{V_1} = \frac{I_1}{I_2}$$


$$S_r = V_{1r} \times I_{1r} = V_{2oc} \times I_{2r}$$

### Condition for Maximum Efficiency


Iron Loss = Copper Loss

$$P_{core} = P_{cu} = R_s I_2^2$$
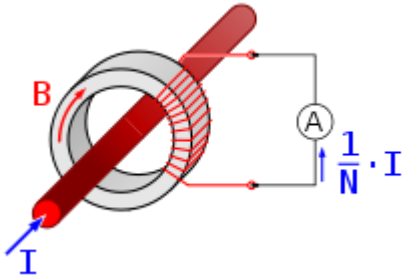
$$I_2 = \sqrt{\frac{P_{core} = P_{cu}}{R_s}}$$



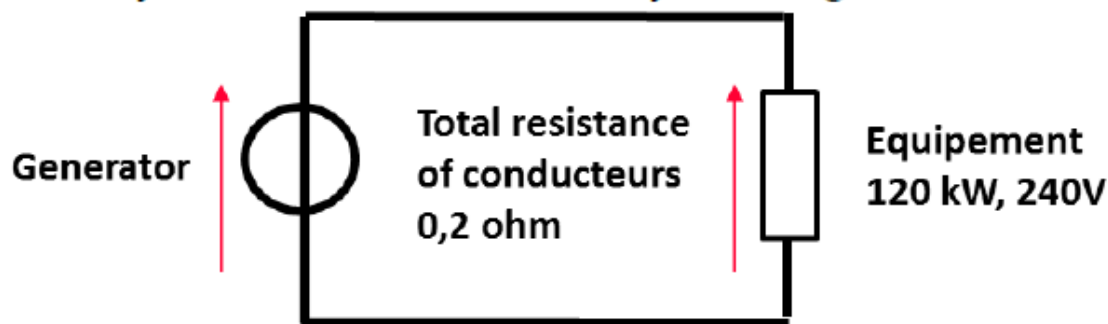**Exercise 1.** A farmer installs a private hydroelectric generator to provide power for equipment rated a  $120\text{ kW}$   $240\text{ V AC}$ . The generator is connected to the equipment by two conductors which have a total resistance of  $0,2\Omega$  -. The system is shown schematically in the figure below.



- a) The equipment is operating at its rate power. Calculate:
- (1) The power loss in the cables;
  - (2) The voltage which must be developed by the generator;
  - (3) The efficiency of the transmission system.

## Solution

(1) The power loss in the cables;

$$P_s = VI \cos \varphi = 240 \times I \times 1 = 120000W$$

$$I = \frac{120000}{240} = 500A$$

$$P_{cable} = RI^2 = 0,2 \times 500^2 = 50kW$$

(2) The voltage which must be developed by the generator;


$$V_{in} = RI + 240 = 0,2 \times 500 + 240 = 340V$$

(3) The efficiency of the transmission system.

$$P_e = P_{cable} + P_L = 50 \times 10^3 + 120 \times 10^3 = 170kW$$

$$\eta = \frac{P_s}{P_e} = \frac{120 \times 10^3}{170 \times 10^3} = 0,705$$

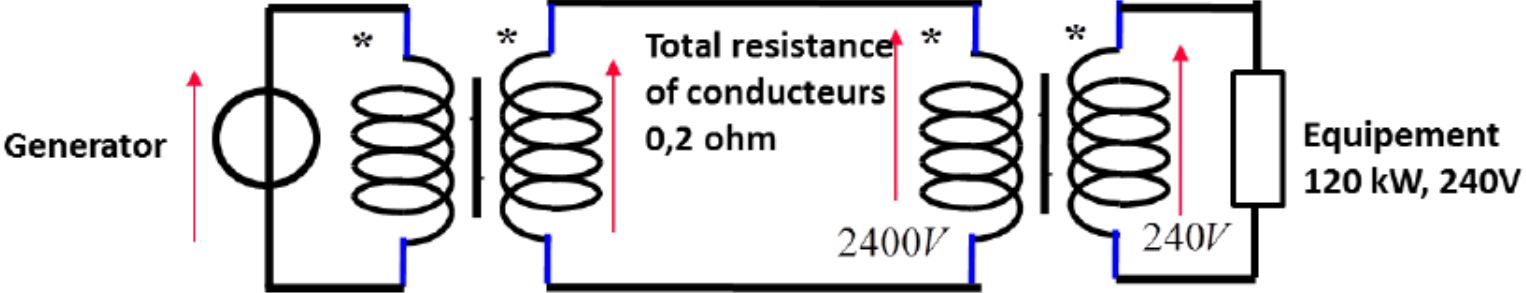b) An engineer suggest that the farmer uses a transformer to convert the generator output to give a  $2400\text{ V}$  at the end of the transmission line, as shown in the next figure. A second transformer is to be used to step down this voltage to  $240\text{ V}$ .



- (4) Explain briefly how a transformer makes use of electromagnetic induction to produce an output voltage several times bigger than the input voltage.
- (5) The transformer is 100 % efficient. Calculate the power loss in the new transmission system.

## Solution

(4) Explain briefly how a transformer makes use of electromagnetic induction to produce an output voltage several times bigger than the input voltage.

There is a direct relationship between voltage, impedance, current, and the number of primary and secondary coil turns in a transformer

$$m = \frac{n_2}{n_1} = \frac{V_{2oc}}{V_1} = \frac{I_1}{I_2}$$

(5) The transformer is 100 % efficient. Calculate the power loss in the new transmission system.

$$\frac{V_{2oc}}{V_1} = \frac{I_1}{I_2} \rightarrow I_1 = \frac{V_{2oc}}{V_1} \times I_2 = \frac{240}{2400} \times 500 = 50A$$

$$P_{cable} = RI^2 = 0,2 \times 50^2 = 500W$$

# Transformateur monophasé 600 kV



# Reminders

- **A transformer is a device which transfers electrical energy (power) from one voltage level to another voltage level.**
- **Unlike in rotating machines, there is no energy conversion.**
- **A transformer is a static device and all currents and voltages are AC.**
- **The transfer of energy takes place through the magnetic field.**

# Transformer Construction

## Iron Core


- **The iron core is made of thin laminated silicon steel (2-3 % silicon)**
- **Pre-cut insulated sheets are cut or pressed in form and placed on the top of each other .**
- **The sheets are overlap each others to avoid (reduce) air gaps.**

# Transformer Construction

## Iron Core
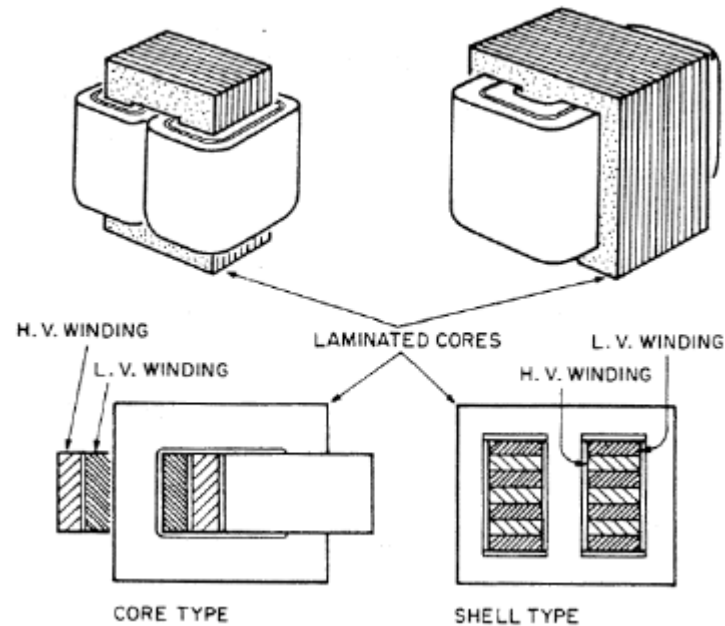
### Small transformer winding

- The windings are manufactured in several layers, and insulation is placed between windings.
- The primary and secondary windings are placed on top of each others but insulated by several layers of insulating sheets.
- The windings are dried in vacuum and impregnated to eliminate moisture.



*The End*